

Open Ended Lab : Explore These circuits by yourself, clearly show your output, procedure and method how you are analyzing these circuits.

